

Building a Breathalyzer with MQ-3 and Arduino

March 7, 2010

During the First Meeting of Electronic Arts in Florianópolis, we built a Breathalyzer using the Alcohol Gas Sensor MQ-3 and an Arduino Board to use in the last day of the meeting, in which we gave a party. You can see a quick video two posts below. Last days I received many emails asking for the code or how to make one, so I decided to build the sensor again, take pictures/videos and make a tutorial showing how you can make one, so here it is.




Parts Needed:

- Arduino Board (http://www.arduino.cc)
- 10x 5mm LEDs (Green, Yellow and Red)
- 100K Ω Potentiometer (to calibrate the sensor)
- $10x \approx 220\Omega$ Resistor (anything between 220Ω and 470Ω is OK)
- BreadBoard




• MQ-3 Sensor from Sparkfun (http://www.sparkfun.com/datasheets/Sensors/MQ-3.pdf)

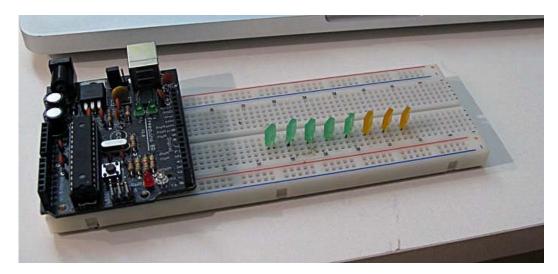
Here are some pictures from the building process:









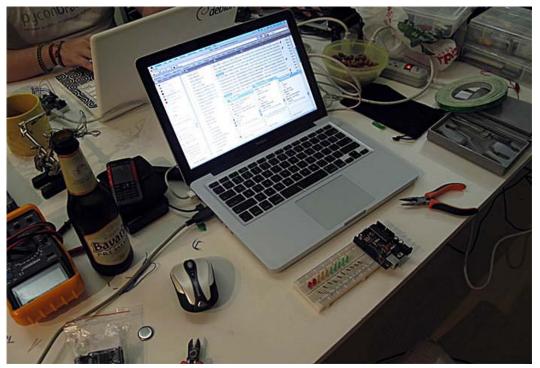

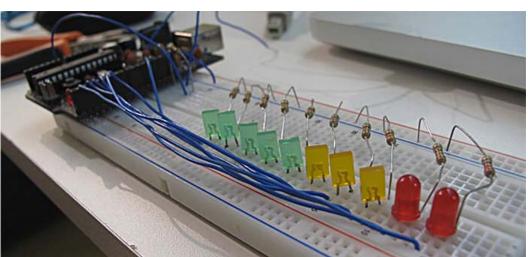


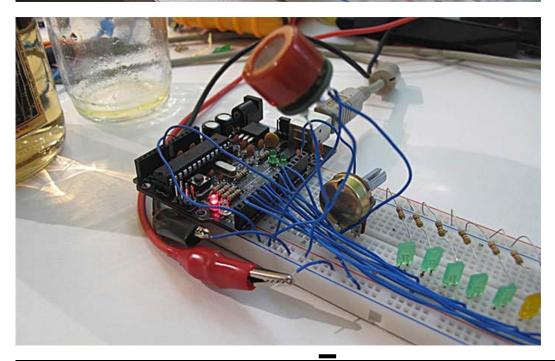

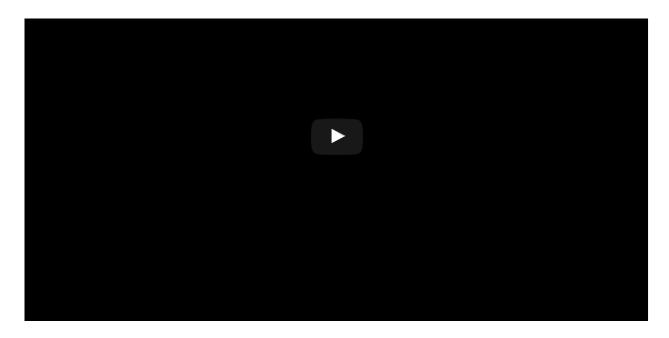


To make the LEDs work, I have connected them in sequence using the Digital Pins 2 till 11 (ten LEDs total). Remember to use a resistor between 220Ω and 470Ω for each LED, like shown on the picture below:

Arduino Digital I/O Pins

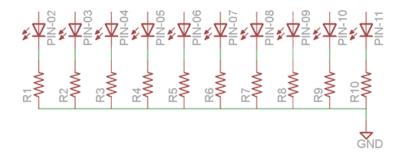


To connect the sensor, you have to connect one of the H pin to +5V Supply (use an external power supply for that, it may be too much current for the arduino) and the other one to Ground.

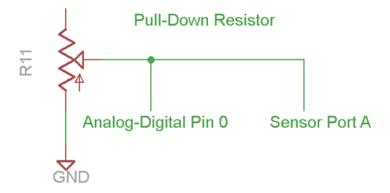Pin B (any of them) you connect to Ground. And the A pin (also any of them) you connect to the $100 \text{K}\Omega$ potentiometer as shown on the picture below. In the same pin where you are connecting the pin A, you need to connect a wire to the Analog/Digital Converter in Arduino, that is where you are going to read the Alcohol information.





MQ-3 Sensor

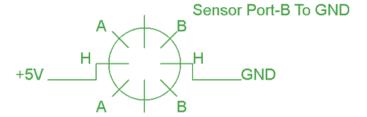

This is a quick and easy DIY project, but if you have any problem building it, please feel free to post questions!

You can DOWNLOAD the .PDE file HERE (http://danielandrade.net/files/breathanalyzer.pde).

```
1
 2
 3
     @ Code for interfacing Alcohol Gas Sensor MQ-3 with Arduino
     @ Code by Daniel Spillere Andrade and Daniel Amato Zabotti
 4
 5
     @ daniel@danielandrade.net / danielzabotti@gmail.com
 6
           www.DanielAndrade.net
 8
 9
10
     const int analogPin = 0;
                                 // the pin that the potentiometer is attached to
11
     const int ledCount = 10;
                                 // the number of LEDs in the bar graph
12
13
     int ledPins[] = {
14
15
       10,9,8,7,6,5,4,3,2,1 // Here we have the number of LEDs to use in the BarGraph
16
       };
17
18
19
     void setup() {
20
       for (int thisLed = 0; thisLed < ledCount; thisLed++) {</pre>
21
22
         pinMode(ledPins[thisLed], OUTPUT);
23
       }}
24
25
     void loop() {
26
       //This is the code to light up LED's
       int sensorReading = analogRead(analogPin);
27
28
       int ledLevel = map(sensorReading, 500, 1023, 0, ledCount);
29
30
31
32
       for (int thisLed = 0; thisLed < ledCount; thisLed++) {
33
         if (thisLed < ledLevel) {</pre>
34
35
           digitalWrite(ledPins[thisLed], HIGH);
36
         }
37
38
         else {
39
           digitalWrite(ledPins[thisLed], LOW);
40
41
       }
42
                 view raw (https://gist.github.com/dansku/5682877/raw/490a44fa60d73f251083dab590d7958e11b65d8e/Breathalyzer.ino)
```

(https://gist.github.com/dansku/5682877#file-breathalyzer-ino) hosted with ♥ by GitHub (https://github.com)